
#### Overview

- ➤ Memory Hierarchy
- Main Memory
- Auxiliary Memory
- Associative Memory
- ➤ Cache Memory
- Virtual Memory

 
## Memory Hierarchy

Memory Hierarchy is to obtain the highest possible access speed while minimizing the total cost of the memory system




### Main Memory

# RAM and ROM Chips Typical RAM chip

 

CS1	CS2	RD	WR	Memory function	State of data bus
0	0	Х	Х	Inhibit	High-impedence
0	1	Х	X	Inhibit	High-impedence
1	0	0	0	Inhibit	High-impedence
1	0	0	1	Write	Input data to RAM
1	0	1	X	Read	Output data from RAM
1	1	Х	Χ	Inhibit	High-impedence

#### Typical ROM chip

 

### Connection of Memory to CPU

RAM chip is better suited for communication with CPU
Control inputs selects the chip only when needed
A bidirectional data bus allows the transfer of data either from memory to CPU
during read /write operation

A bidirectional bus is made of Tri state buffer

The capacity of memory is 128 words of 8 bits

It requires 7 Bit address and 8 bit bidirectional data bus

The unit is operational only when CS1=0 and bar CS2=0

The small x's under the address bus lines designate those line that must be connected to the address inputs in each chip

### Memory Address Map

#### Address space assignment to each memory chip

Example: 512 bytes RAM and 512 bytes ROM

	Неха	Address bus									
Component	address	10	9	8	7	6	5	4	3	2	1
RAM 1	0000 - 007F	0	0	0	х	Х	х	Х	х	х	х
RAM 2	0080 - 00FF	0	0	1	X	X	X	X	X	X	X
RAM 3	0100 - 017F	0	1	0	X	X	X	X	X	X	X
RAM 4	0180 - 01FF	0	1	1	X	X	X	X	X	X	X
ROM	0200 - 03FF	1	X	X	X	X	X	X	X	X	X

#### **Memory Connection to CPU**

- -RAM and ROM chips are connected to a CPU through the data and address buses
- -- The low-order lines in the address bus select the byte within the chips and other lines in the address bus select a particular chip through its chip select inputs

### Connection of Memory to CPU

